

Year 2 2023/2024



Choose the correct answer:

- 1. A circuit is a path for the ------ to move along and make things work. (electricity - water)
- 2. The ------ shines when it is in a complete circuit. (cell lamp)
- 3. Electricity moves through ------. (wires wood)
- 4. In a circuit, each cell has ------ connections and both are used. (four- two)
- 5. The ------ holds the cell and connects it to the wires. (cell holder- lamp holder)
- 6. A cell is often called a -----. (wire- battery)
- 7. Electricity moves through the ----- part of a wire. (metal- plastic)
- 8. The lamp holder holds the ------ and connects it to the wires. (cell- lamp)
- 9. ------ is a conductor of electricity. (Plastic- Metal)

Draw a circle around the circuits that will work:



