
Model answer of revision pack

1
$$A_2 = 2.5 (A)$$

$$A_3 = 2.5 (A)$$

- 2 a To measure the current in the lamp, an ammeter is connected in series with the lamp.
 - **b** To measure the voltage across the lamp, **a voltmeter** is connected **in parallel** with the lamp.
- 3 a 1.5 (V)
- 4 voltage = current x resistance or V = IR or 2×10 Answer = 20 (V)
- 5 circuit drawn with 1 cell, 1 lamp and 1 buzzer in parallel with a switch on each branch variable resistor in series with the lamp no gaps at corners and no wires drawn through or into components

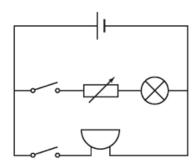

- **1** Ω
- 2 It makes it more difficult for current to flow.
- **3** Voltage / V in top of triangle; current / I at the bottom right.

Ohm's law

c i resistance =
$$\frac{\text{voltage}}{\text{current}} = \frac{6}{2} = 3\Omega$$

ii current =
$$\frac{\text{voltage}}{\text{resistance}} = \frac{12}{3} = 4 \text{ A}$$

- a) Particles of the air (gas) collide with the walls of the tyres causing a force on these walls
- b) increase
 particles have more energy, so they move faster
 making more collisions with the walls which
 makes a greater force
- a) The pressure increases
- b) The pressure decreases
- c) Particles of the air (gas) collide with the sides of the beaker causing a force on these sides

Mike is half the weight of Oliver & Mike is twice as far from the pivot than Oliver.

Mike's moment is 500 × 2 or 1000 (Nm)

Oliver's moment is 1000 × 1 or 1000 (Nm)

So, Mike's moment is equal to Oliver's moment

b) i) Moment = Force x Distance = 50 x 0.3 = 15 Nm

Distance-time graph:

a) Average speed = Total distance/Total time = 300/15 = 20 m/s

b) Stops / At rest

c) Returns back to the starting point d) faster

- 1 It contains a branch / there is more than one path for the current to flow / each component is connected across the battery.
- 2 a 3+2=5 A
 - **b** $(A_1 =) A_2 + A_3$
- 3 a 12 V
 - **b** 12 V
 - a) Because the forces are equal (balanced)
 - b) The force from James decreased (became less)